
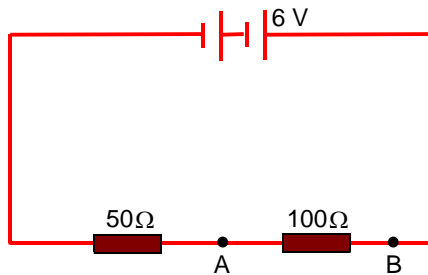

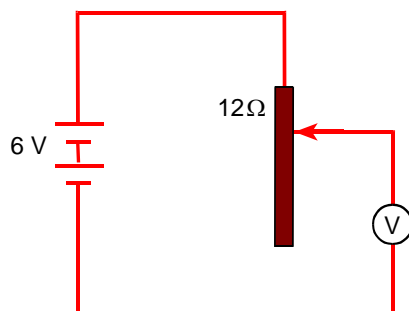
## TAP 118- 2: Tapping off a potential difference




A series circuit is connected as shown in the diagram.

1. What is the potential difference between A and B?
2. An additional resistor of  $100\Omega$  is connected between the  $50\Omega$  resistor and the cells. What is the potential difference between A and B now?
3. The additional  $100\Omega$  resistor is now connected in parallel with the first  $100\Omega$  resistor. What is the potential difference between A and B now?
4. A potential divider is made from a  $4\text{ k}\Omega$  and a  $6\text{ k}\Omega$  resistor connected in series with a  $20\text{ V}$  supply. Draw a diagram of the arrangement. What four values of potential difference can be tapped off?
5. A student puts a  $12\Omega$  variable resistor in series with a  $6\text{ V}$  battery, expecting to get a variable potential difference.



The voltmeter is a high resistance digital multimeter. Explain why the circuit won't work. Draw a circuit which would work.

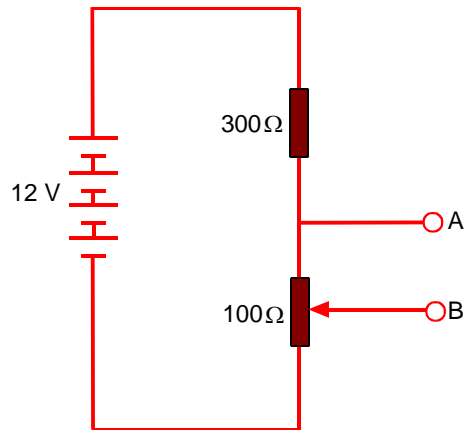6. B is the wiper of a  $100\ \Omega$  rotary potentiometer.



What is the full range of the potential difference that can be tapped off between A and B?

### Hints

1. Resistors are in the ratio  $50 : 100$  so the potential difference splits up  $1 : 2$ .
3. Work out the equivalent resistance of the two  $100\ \Omega$  resistors in parallel first.
6. Find the pd set up across the potentiometer first by looking at the ratio of the resistors.

## Answers and worked solutions

1.  $100\ \Omega / (50\ \Omega + 100\ \Omega) \times 6\ \text{V} = 4\ \text{V}$
2.  $100\ \Omega / (50\ \Omega + 100\ \Omega + 100\ \Omega) \times 6\ \text{V} = 2.4\ \text{V}$
3. Resistance of parallel combination =  $50\ \Omega$ . So the  $6\ \text{V}$  supply potential difference splits equally between the two  $50\ \Omega$  and pd across AB is  $3\ \text{V}$ .
4. Resistance of whole potential divider is  $10\ \text{k}\Omega$

$$\text{p.d. across } 4\ \text{k}\Omega = \frac{4\ \text{k}\Omega}{10\ \text{k}\Omega} \times 20\ \text{V} = 8\ \text{V}$$

$$\text{p.d. across } 6\ \text{k}\Omega = \frac{6\ \text{k}\Omega}{10\ \text{k}\Omega} \times 20\ \text{V} = 12\ \text{V}$$

$$\text{p.d. across } 10\ \text{k}\Omega = \frac{10\ \text{k}\Omega}{10\ \text{k}\Omega} \times 20\ \text{V} = 20\ \text{V}$$

5. The resistance has been connected as a variable resistor. The multimeter has an extremely high resistance so that wherever one moves the sliding contact the pd is set up across the voltmeter which always reads  $6\ \text{V}$ ! The redrawn diagram should show the ends of the resistance connected across the battery
6. The resistance of whole potential divider is  $400\ \Omega$ . The supply pd  $12\ \text{V}$  splits between the fixed  $300\ \Omega$  resistor and the  $100\ \Omega$  potentiometer in the ratio of their resistances. So there will be  $9\ \text{V}$  across  $300\ \Omega$  and  $3\ \text{V}$  across  $100\ \Omega$ .

When the slide contact from B is next to A the pd tapped between A and B is  $0\ \text{V}$ ;  
when the slide is at the other end of the potentiometer the full pd of  $3\ \text{V}$  is across AB.

## External references

This activity is taken from Advancing Physics Chapter 2, 170S